


Computer Architecture

Lecture 4



Agenda

- **Part 1: ALU**
 - Types of ALU Micro-operations
 - ALU Design
- **Part 2: Instruction Set Architecture**
 - MIPS Instruction Set Architecture

 


Part 1: ALU

- Types of ALU Micro-operations
- ALU Design



Types of ALU Micro-operations


Types of ALU micro-operations

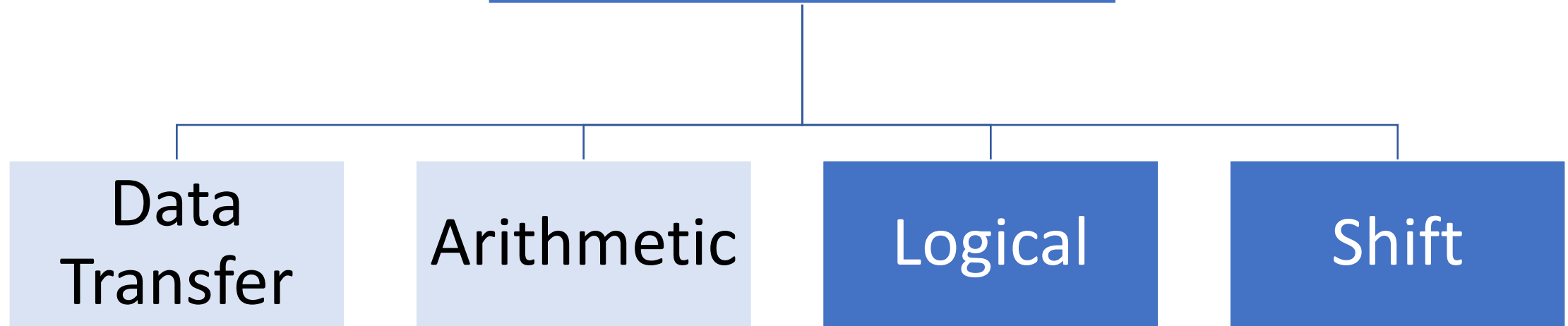

$D \leftarrow A$



Full adder block diagram

 

Inputs			Outputs	
A	B	C _{in}	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table of Full Adder




Types of ALU Micro-operations (Arithmetic micro-operations)

- Addition:

$$D \leftarrow A + B$$

A	0011
+ B	0010

D	0101


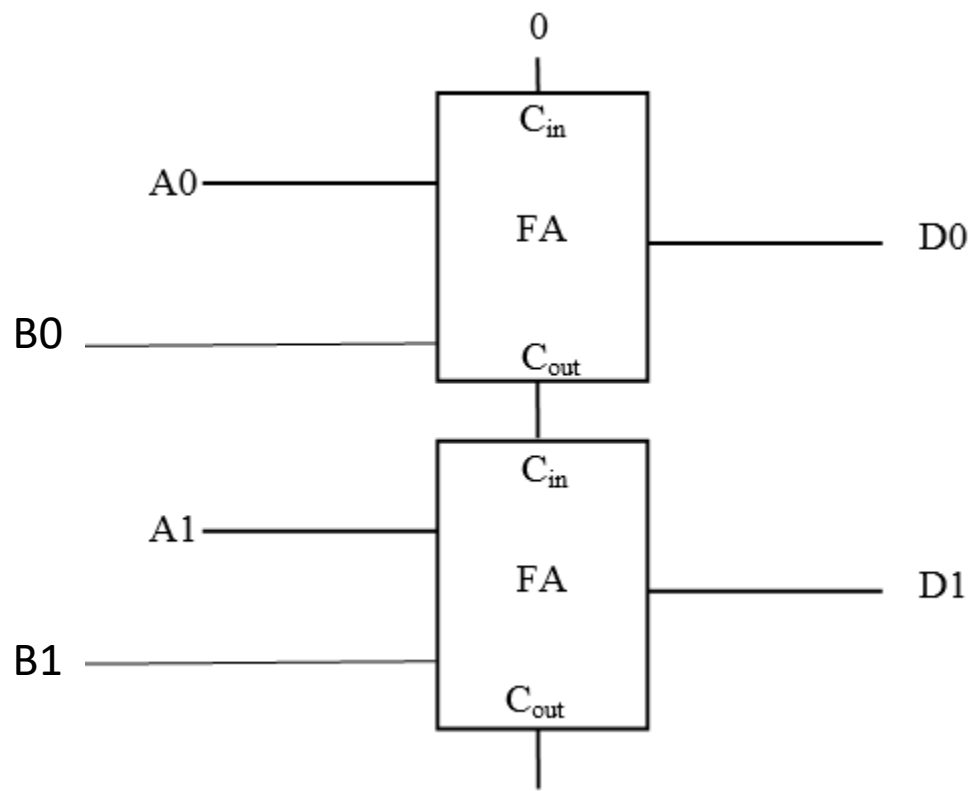




Part 3: Types of ALU Micro-operations (Arithmetic micro-operations)

- Increment:
 $D \leftarrow A + 1$

A	0011
	0001
<hr/>	
D	0100

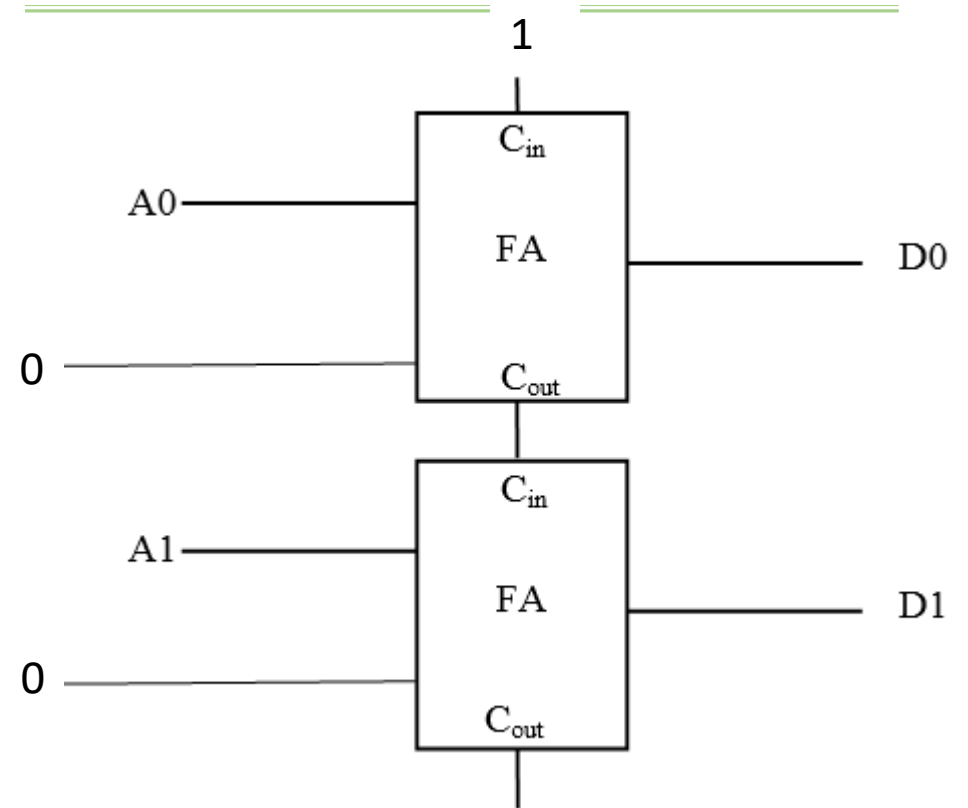 



Part 3: Types of ALU Micro-operations (Arithmetic micro-operations)

- Decrement:

$$D \leftarrow A - 1$$



$\overset{\textcircled{1}}{A} \quad 0101$
 $\quad \quad \quad \textcircled{1111}$
 $\quad \quad \quad \text{-----}$
 $D \quad 0100$

0001

1110
 + 1

1111

- 2's complement OF 1 IS ALL ONES

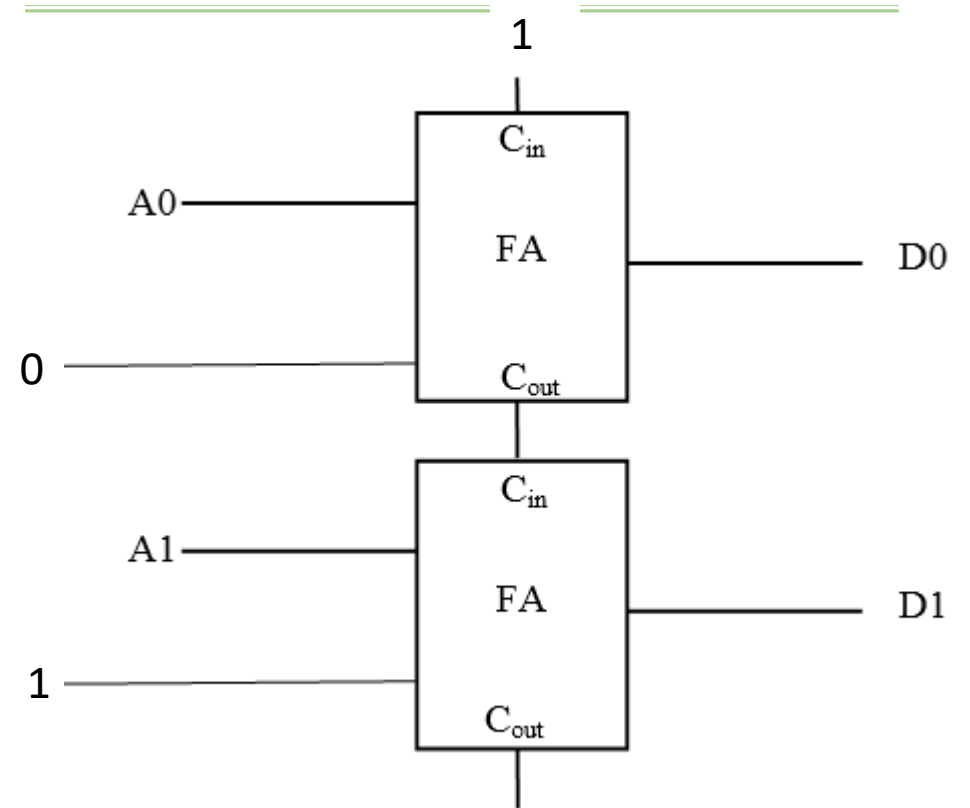 



Part 3: Types of ALU Micro-operations (Arithmetic micro-operations)


0011

- Subtraction:

$$D \leftarrow A + \overline{B} + 1$$

$$\begin{array}{r} 5 \quad 0101 \\ - 3 \quad 0011 \\ \hline \end{array}$$

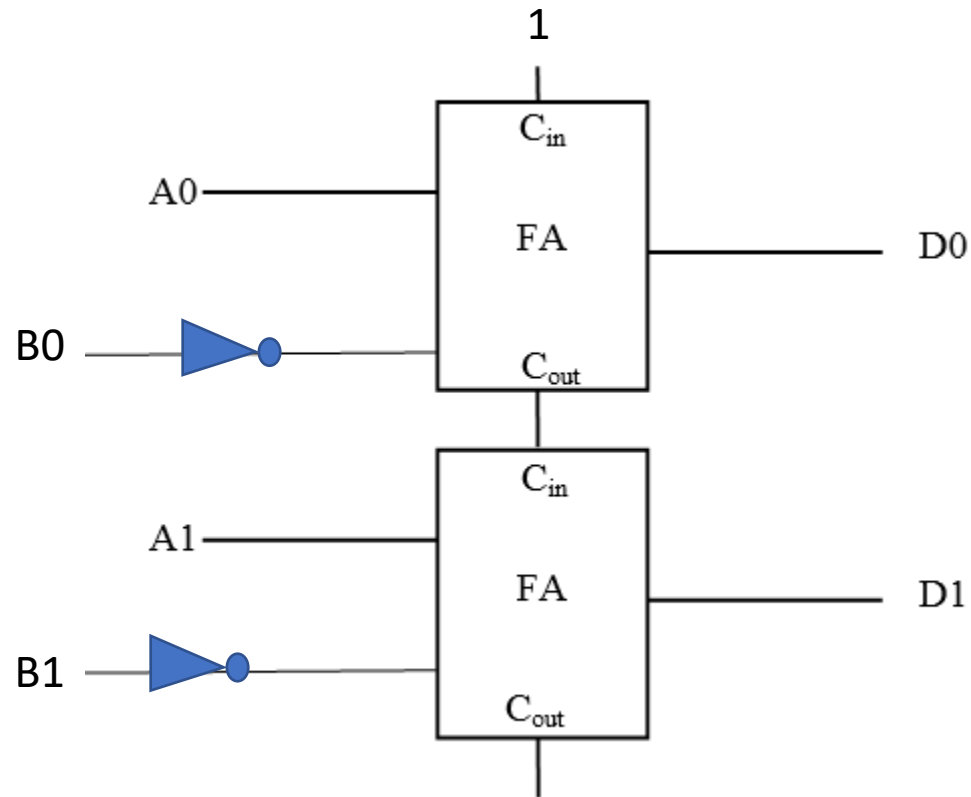- Has to be converted to $5 + (-3)$.
- We have to get negative representation of 3 by applying 2's complement



$$\begin{array}{r} 1's \text{ complement } 1100 \\ + \quad 1 \\ \hline 1101 \end{array}$$

- 2's complement, this is -3





ALU design for Arithmetic micro-operations

How the ALU is designed to allow all the arithmetic microoperations?



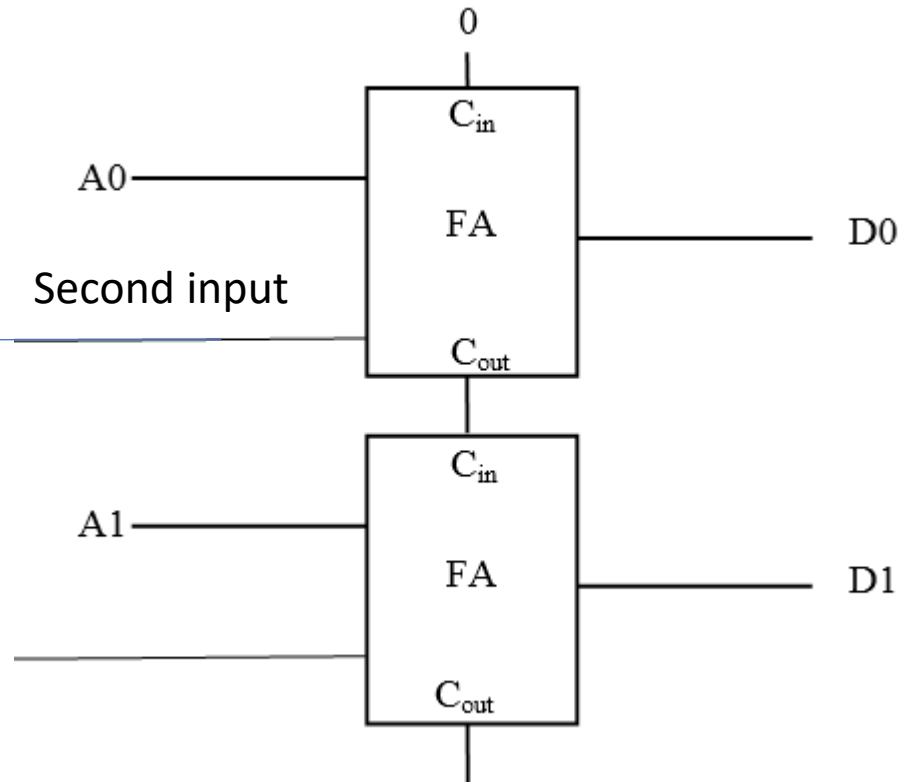 The choice of the second input specifies the micro-operation performed






Note the C_{in} has also an impact on the micro-operation

Select			Input Y	Output $D = A + Y + C_{in}$	Microoperation
S_1	S_0	C_{in}			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\bar{B}	$D = A + \bar{B}$	Subtract with borrow
0	1	1	\bar{B}	$D = A + \bar{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

4-bit arithmetic circuit

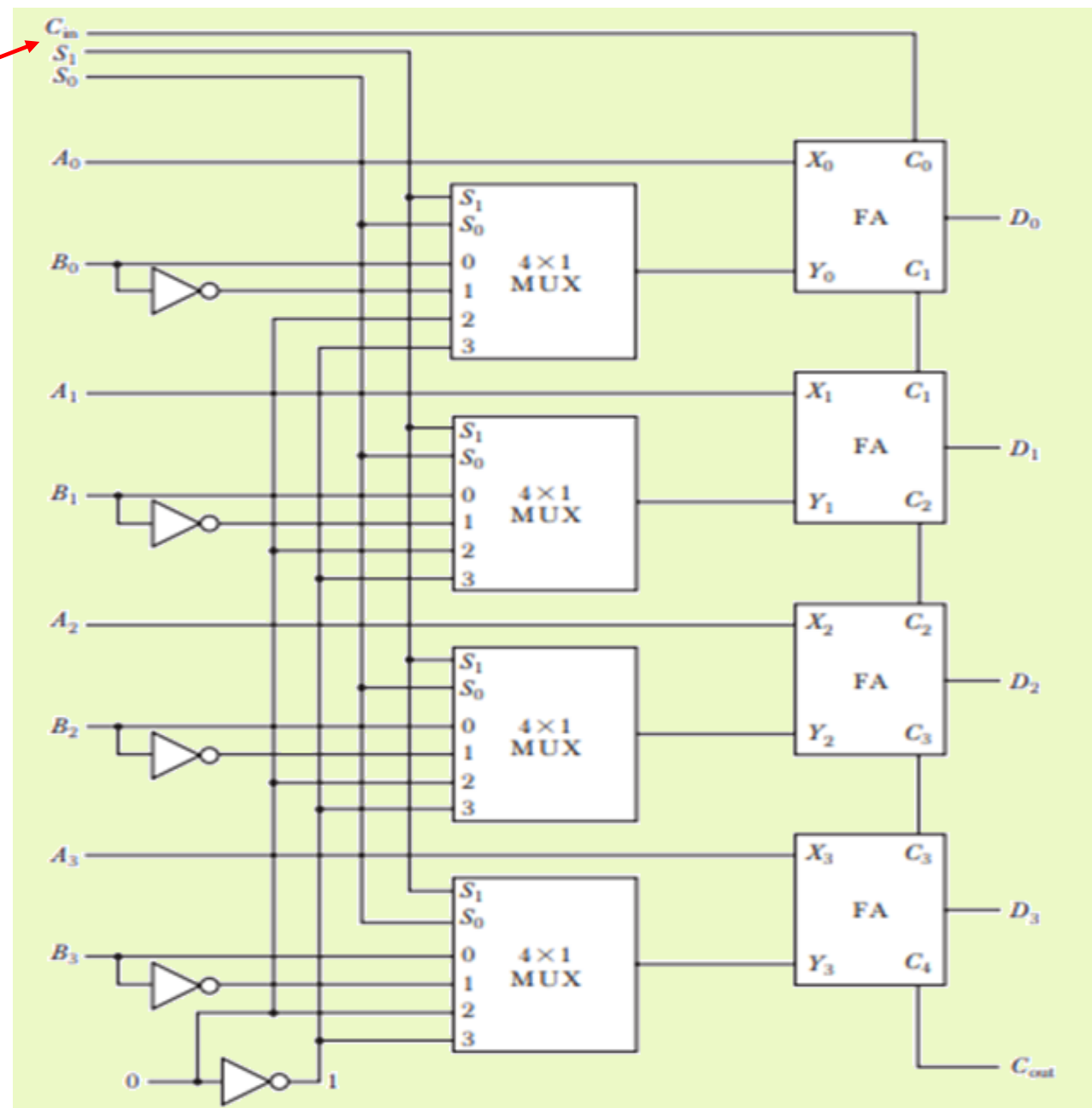


4-bit arithmetic circuit



Types of ALU micro-operations

Types of ALU micro-operations

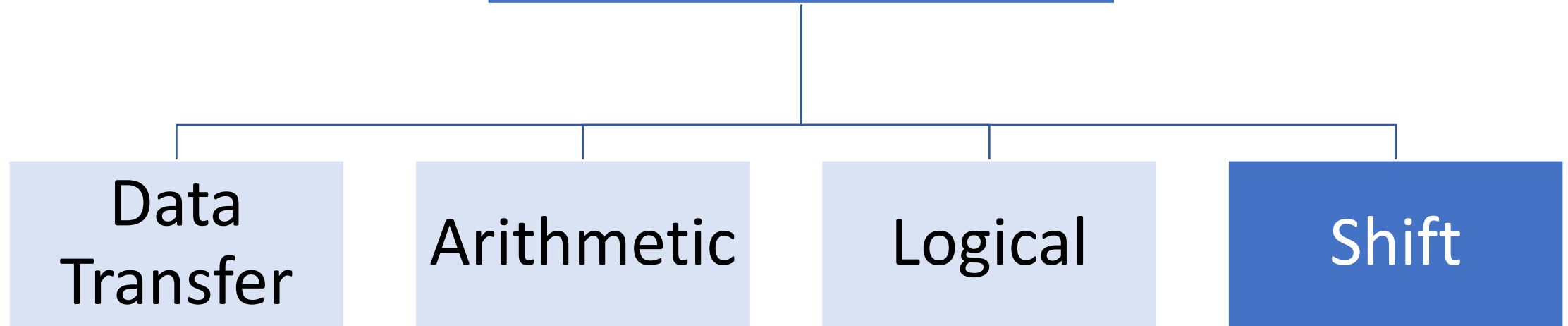

Data
Transfer

$D \leftarrow A$

Arithmetic

$D \leftarrow A+B$

$D \leftarrow A+B'+1$

$D \leftarrow A+1$

$D \leftarrow A-1$

Logical

Shift



Logical Micro-operations

Four Logical micro-operations


S1	S0	
0	0	$E \leftarrow A \wedge B$ (And)
0	1	$E \leftarrow A \vee B$ (OR)
1	0	$E \leftarrow A \oplus B$ (XOR)
1	1	$E \leftarrow A'$ (NOT)

$$\begin{array}{r}
 \wedge \quad A \quad 0110 \\
 \quad B \quad 0101 \\
 \hline
 E \quad 0100
 \end{array}$$

$$\begin{array}{r}
 \vee \quad A \quad 0110 \\
 \quad B \quad 0101 \\
 \hline
 E \quad 0111
 \end{array}$$

$$\begin{array}{r}
 \oplus \quad A \quad 0110 \\
 \quad B \quad 0101 \\
 \hline
 E \quad 0011
 \end{array}$$
 
$$\begin{array}{r}
 A \quad 0110 \\
 \hline
 E \quad 1001
 \end{array}$$



One stage of the logical circuit



Shift micro-operations

Shift Micro-operations

$$V_s = R_{n-1} \oplus R_{n-2}$$

Logical Shift
left

Logical Shift
right

Circulate
left

Circulate
right

Arithmetic
Shift left

Arithmetic
Shift right

Example1
←
0010
↙ ↘
0100

→
0100
↙ ↘
0010

←
0101
↙ ↘
1010

→
0101
↙ ↘
1010

←
0010
↙ ↘
0100 $V_s = 0$

→
0100
↙ ↘
0010

Example2
1010
↙ ↘
0100

1100
↙ ↘
0110

1100
↙ ↘
1001

1100
↙ ↘
0110

1010
↙ ↘
0100 $V_s = 1$

1100
↙ ↘
1110

1 Shift left → multiply
by 2 with unsigned
numbers

1 Shift right → divide
by 2 with unsigned
numbers

Can not solve the problem,
but indicates overflow



Check your Understanding

Problem:

Starting from an initial value of $R = 01101001$, determine the sequence of binary values of R after a logical shift left, followed by a circular shift right, followed by an arithmetic shift right, followed by arithmetic shift left. State whether there is an overflow.



Solution:

$R = 01101001$


After logical Shift left: 11010010

After circular shift right: 01101001

After arithmetic Shift right: 00110100

Arithmetic shift left: 01101000

 After arithmetic shift left, no overflow occurred.





Shift micro-operations

RTL	Description
$R \leftarrow \text{shl } R$	Shift Left register R
$R \leftarrow \text{shr } R$	Shift right register R
$R \leftarrow \text{cil } R$	Circular shift Left register R
$R \leftarrow \text{cir } R$	Circular shift right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift Left register R
$R \leftarrow \text{ashr } R$	Arithmetic shift right register R



Shift micro-operations


Shifting left

A3	A2	A1	A0	Before Shifting left
A2	A1	A0	Input	After Shifting left

Shifting right

A3	A2	A1	A0	Before Shifting right
Input	A3	A2	A1	After Shifting right


S	H3	H2	H1	H0	Micro-operation
0	A3	A1	A0	I _R	Shift left
1	I _L	A3	A2	A1	Shift right

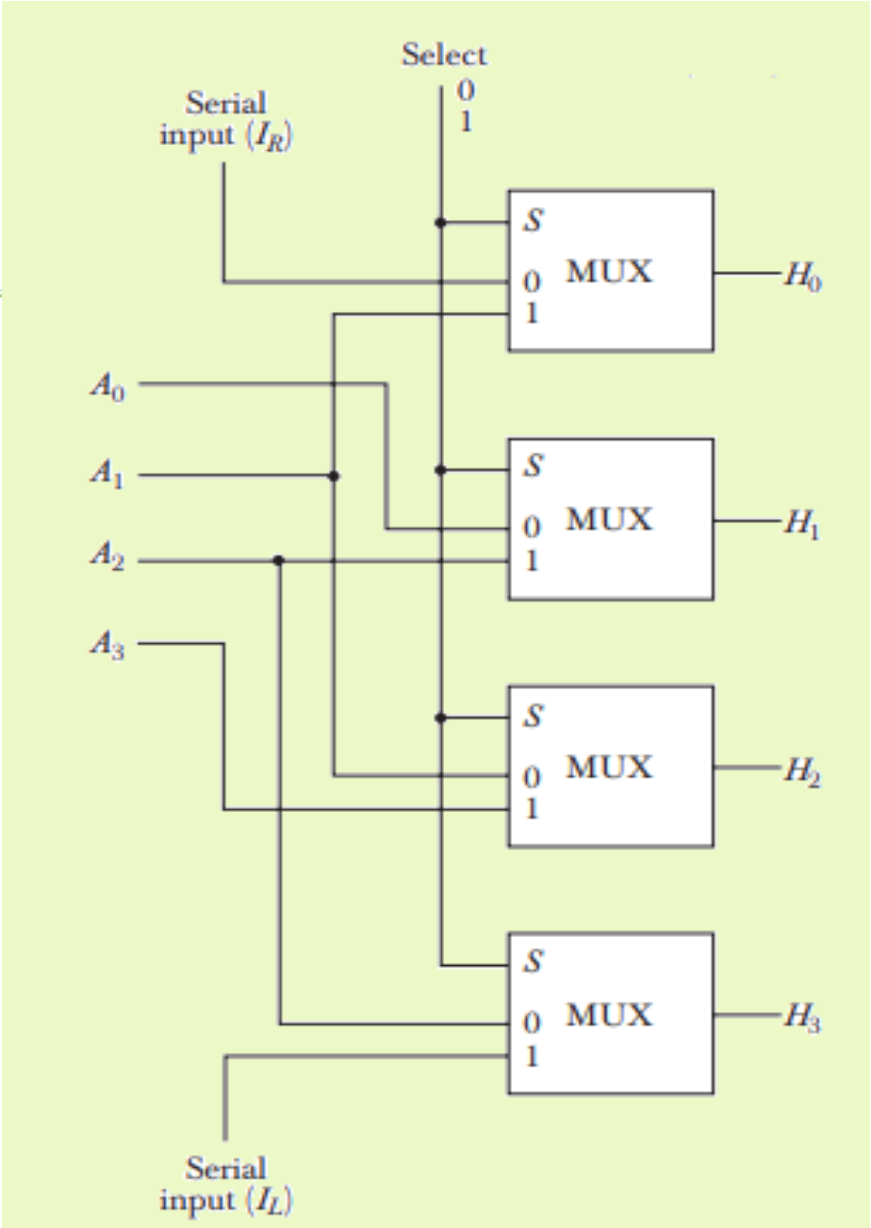


4-bit circuit shifter



One Stage of ALU

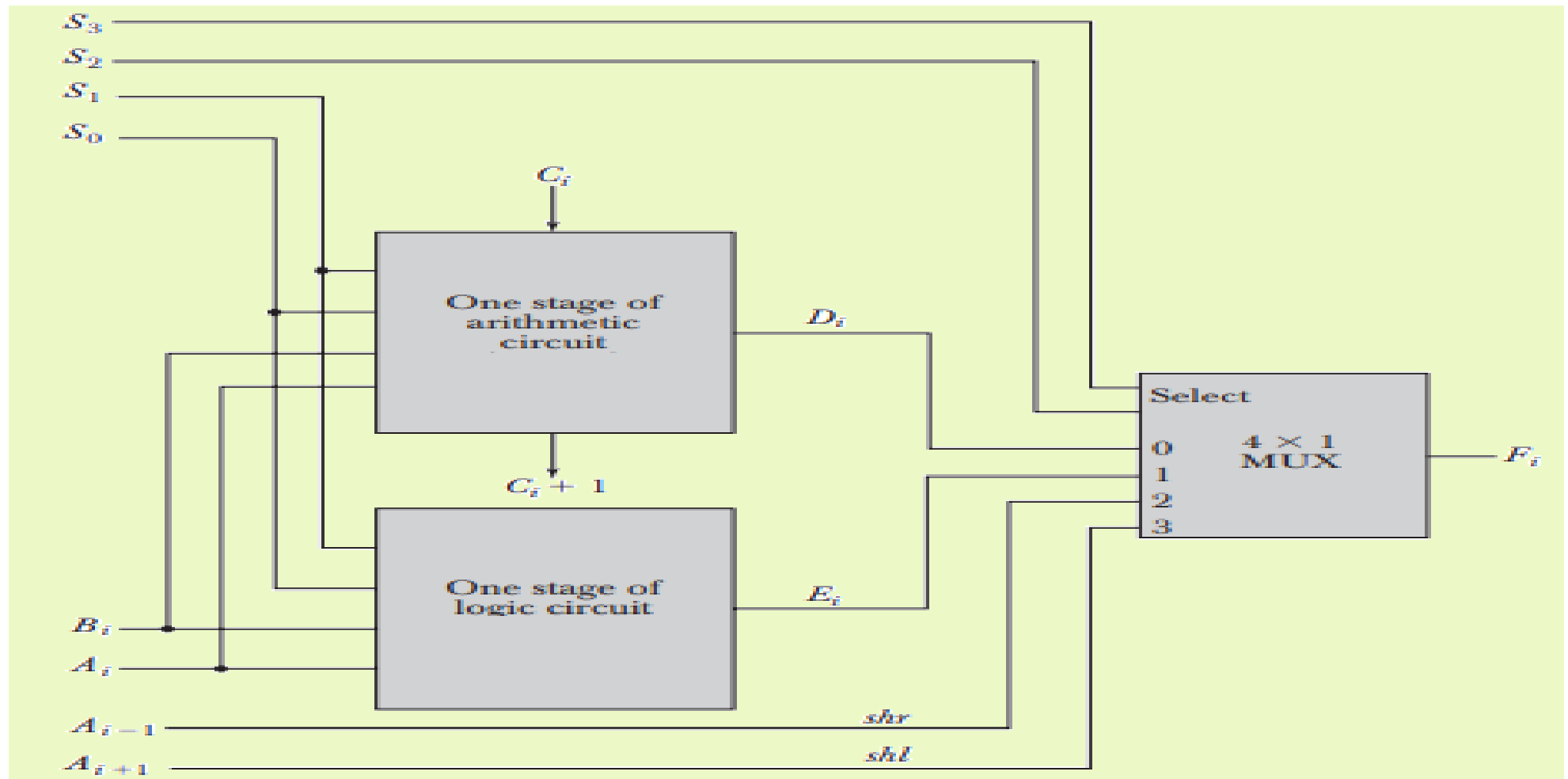

 

Part 2: Instruction Set Architecture

- MIPS ISA



Instruction Set Architecture

- An Instruction Set Architecture (ISA) is part of the abstract model of a computer that defines how the CPU is controlled by the software.
- The ISA acts as an interface *between the hardware and the software*, specifying both what the processor is capable of doing as well as how it gets done.



Instruction Set

- An instruction set is a group of commands for a central processing unit (CPU) in machine language. The term can refer to all possible instructions for a CPU or a subset of instructions to enhance its performance in certain situations.

**We will study
MIPS microprocessor
Its Instruction Set Architecture and
Its Instruction Set**





MIPS microprocessor

The five most iconic devices using MIPS CPUs



**Sony PlayStation
(MIPS R3000 CPU)**



Nintendo 64 (MIPS R4300i CPU)



Tesla Model S (MIPS I-class CPU)



**NEC Cenju-4 (MIPS R10000 CPU)
supercomputer**



**SGI Indigo (MIPS R3000)
workstation**



MIPS-32 ISA

- MIPS-32 uses 32 general purpose registers, each 32 bits wide
- The MIPS architecture can support up to 32 address lines.
- MIPS is a byte-addressable architecture
- The word size is 32-bits




MIPS commonly used registers

Register Number	Register Name	Description
0	\$zero	The value 0
2-3	\$v0 - \$v1	(values) from expression evaluation and function results
4-7	\$a0 - \$a3	(arguments) First four parameters for subroutine
8-15, 24-25	\$t0 - \$t9	Temporary variables
16-23	\$s0 - \$s7	Saved values representing final computed results
31	\$ra	Return address



Categories of MIPS instructions

 




Arithmetic instructions

add \$s2, \$s1, \$s0


**destination
register**

**Source operand
registers**


\$s0

 

\$s1

 

\$s2

 

sub \$s2, \$s0, \$s1

\$s2 = 2

mul \$s2, \$s1, \$s0

\$s2 = 15

div \$s2, \$s0, \$s1

\$s2 = 1




Arithmetic instruction

`addi $s2, $s1, 3`

destination register (points to `$s2`)


Source operand register (points to `$s1`)

Immediate value (points to `3`)

 

`li $s4, 50`

 Data transfer instruction (points to `li`)






MIPS Assembly Example

```
a = 5  
b = 3  
c = 10  
x = a+b  
y = x+7  
x = y- a  
z= c * x  
result = z/a
```

```
li $s0, 5  
li $s1, 3  
li $s2, 10  
add $t0, $s0, $s1  
addi $t1, $t0, 7  
sub $t0, $t1, $s0  
mul $t3, $t0, $s2  
div $s3, $t3, $s0
```



```
# Declare main as a global function
.globl main
# All program code is placed after the
# .text assembler directive
.text

# The label 'main' represents the starting point
main:
    li $s0, 5
    li $s1, 3
    li $s2, 10
    add $t0, $s0, $s1
    addi $t1, $t0, 7
    sub $t0, $t1, $s0
    mul $t3, $t0, $s2
    div $s3, $t3, $s0
    li $v0, 10 # Sets $v0 to "10" to select exit syscall
    syscall # Exit
```

```
R0    [r0] = 0
R1    [at] = 0
R2    [v0] = 10
R3    [v1] = 0
R4    [a0] = 7
R5    [a1] = 2147481548
R6    [a2] = 2147481580
R7    [a3] = 0
R8    [t0] = 10
R9    [t1] = 15
R10   [t2] = 0
R11   [t3] = 100
R12   [t4] = 0
R13   [t5] = 0
R14   [t6] = 0
R15   [t7] = 0
R16   [s0] = 5
R17   [s1] = 3
R18   [s2] = 10
R19   [s3] = 20
```




Thank You

